

Ayden Dauenhauer, Edward Park  
Prof. Yang  
ECEN 122L Tuesday 2:15 p.m.  
23 January 2024

## Lab 2 - State Machine Control of Simple Datapath

### Verilog Code:

/\* output state logic

input: state

output: 8 control signals

TODO: you need to complete the output logic in the following always statement

\*/

```
always@(*)
begin
  case(state)
    IDLE:
      begin
        _Extern = 1'b0;
        Gout = 1'b0;
        Ain = 1'b0;
        Gin = 1'b0;
        RdX = 1'b0;
        RdY = 1'b0;
        WrX = 1'b0;
        add_sub = 1'b0;
      end
    LOAD:
      begin
        _Extern = 1'b1;
        Gout = 1'b0;
        Ain = 1'b0;
        Gin = 1'b0;
        RdX = 1'b0;
        RdY = 1'b0;
        WrX = 1'b1;
        add_sub = 1'b0;
      end
    READ_Y:
      begin
        _Extern = 1'b0;
        Gout = 1'b0;
```

```

        Ain = 1'b1;
        Gin = 1'b0;
        RdX = 1'b0;
        RdY = 1'b1;
        WrX = 1'b0;
        add_sub = 1'b0;
    end
READ_X:
    begin
        _Extern = 1'b0;
        Gout = 1'b0;
        Ain = 1'b1;
        Gin = 1'b0;
        RdX = 1'b1;
        RdY = 1'b0;
        WrX = 1'b0;
        add_sub = 1'b0;
    end
ADD:
    begin
        _Extern = 1'b0;
        Gout = 1'b0;
        Ain = 1'b0;
        Gin = 1'b1;
        RdX = 1'b1;
        RdY = 1'b0;
        WrX = 1'b0;
        add_sub = 1'b0;
    end
SUB:
    begin
        _Extern = 1'b0;
        Gout = 1'b0;
        Ain = 1'b0;
        Gin = 1'b1;
        RdX = 1'b0;
        RdY = 1'b1;
        WrX = 1'b0;
        add_sub = 1'b1;
    end
end

```

```

MV:
begin
    _Extern = 1'b0;
    Gout = 1'b0;
    Ain = 1'b0;
    Gin = 1'b1;
    RdX = 1'b0;
    RdY = 1'b0;
    WrX = 1'b0;
    add_sub = 1'b0;
end
WRITE_X:
begin
    _Extern = 1'b0;
    Gout = 1'b1;
    Ain = 1'b0;
    Gin = 1'b0;
    RdX = 1'b0;
    RdY = 1'b0;
    WrX = 1'b1;
    add_sub = 1'b0;
end
DONE:
begin
    _Extern = 1'b0;
    Gout = 1'b0;
    Ain = 1'b0;
    Gin = 1'b0;
    RdX = 1'b0;
    RdY = 1'b0;
    WrX = 1'b0;
    add_sub = 1'b0;
end
endcase
end

```

/\* Next state logic combined with flip-flops

input: clk, execute (stop/go signal), operation (opcode)

output: state

TODO: you need to complete this Next state logic (combined with flip-flops) in the following always statement

```
*/
always@(posedge clk)
begin

case(state)
  IDLE: begin
    if(execute == 1 && operation == 0) state <= LOAD;
    if(execute == 1 && operation == 1) state <= READ_Y;
    if(execute == 1 && operation == 3) state <= READ_Y;
    if(execute == 1 && operation == 2) state <= READ_X;
  end

  LOAD: begin
    state <= DONE; // always go to the DONE state at the next clock tick
  end

  READ_Y: begin
    if(execute == 1 && operation == 1) state <= MV;
    if(execute == 1 && operation == 3) state <= ADD;
  end

  READ_X: begin
    if(execute == 1) state <= SUB;
  end

  ADD: begin
    if(execute == 1) state <= WRITE_X;
  end

  SUB: begin
    if(execute == 1) state <= WRITE_X;
  end

  MV: begin
    if(execute == 1) state <= WRITE_X;
  end

  WRITE_X: begin
```

```

        if(execute == 1) state <= DONE;
    end

```

```

DONE: begin

```

```

    //back to idle if execute back to low
    if(execute == 0) state <= IDLE;

```

```

end

```

```

default: state <= IDLE;

```

```

endcase


```

```


end //end always

```


## Load Simulation:

 


Move Simulation:

 

Add Simulation:

 

## Sub Simulation:

 

## Questions:

1. What problems did you encounter while implementing and testing your system?

Some of the simulations were incorrect and had wrong simulation results. To fix this, we changed the values of the variables.

2. Did any problems arise when demonstrating for the TA? In other words, did the TA ask you to demonstrate something that you did not think of yourself? What was the scenario that you were asked to demonstrate? Provide some thoughts about why you didn't think of this yourself.

We were asked to explain the inputs and outputs based on the simulation waveform. We did not think of this ourselves because our main focus was on the variables. With a quick rundown on how to read the waveform generators inputs and outputs, we were able to explain the add and subtract commands.

3. In this design, the value 0 is readily available by causing both read signals to be deasserted. If the design did not have that capability, what could you have done to implement the move operation? Note that the answer here will likely involve multiple operations, which is fine.

There could be multiple ways of doing this. The first is adding an AND gate with zero, from register 0. Since any value with an AND gate and a zero will give us 0, this will yield us a zero when we need to. Another method could be adding an XOR gate with itself since XOR only gives 1 when the two values are different. When we send in the same value in the XOR gate, it will give us an 0.